


Boolean Logic

Steven R. Bagley


Introduction

- Last week, looked inside a computer...
- Saw how information is represented in binary as digital signals
- Understand how to manipulate those signals
- To do useful things...

Logic Gates

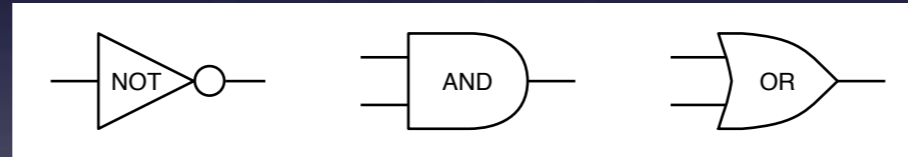


Logic Gates

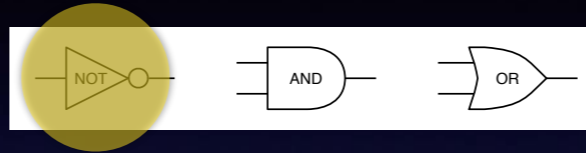


A	Result
0	1
1	0

Logic Gates

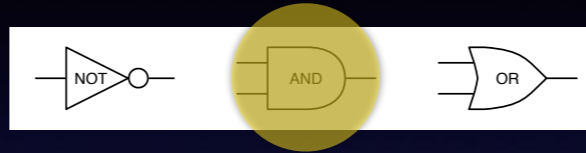

A	B	Result
0	0	0
0	1	0
1	0	0
1	1	1

Logic Gates

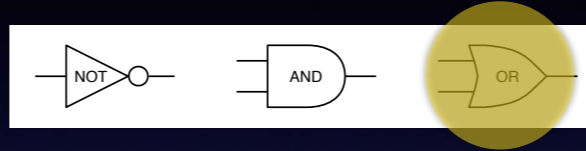

A	B	Result
0	0	0
0	1	1
1	0	1
1	1	1

Logic Functions

- Every boolean function can be expressed using the And, Or and Not functions
- This is called it's *canonical representation*
- And, Or and Not have their own symbols that can be used to write down logic equations
- Similar to how we write down mathematical equations

Unfortunately there are lots of symbols used...

Logic Equations

- Often need to write logic equations down
- Different disciplines use different operators
- AND — $A \wedge B$, $A \& B$, $A \bullet B$
- OR — $A \vee B$, $A | B$, $A + B$
- NOT — $\neg A$, $\sim A$, \overline{A}

Symbols in order, Maths, Programming languages (specifically, C), electronics?
Bar can be extend over other things to show what's inverted
Not C also uses ! in some cases to mean inversion

Precedence

- Operators have precedence
- NOT binds most tightly
- Then AND
- Finally OR
- So $A+B \cdot C$ is equivalent to $A+(B \cdot C)$

Two input functions

Function	A	0	0	1	1
	B	0	1	0	1
Constant Zero	0	0	0	0	0
And	$A \cdot B$	0	0	0	1
A And Not B	$A \cdot \bar{B}$	0	0	1	0
A	A	0	0	1	1
Not A And B	$\bar{A} \cdot B$	0	1	0	0
B	B	0	1	0	1
Xor	$A \cdot \bar{B} + \bar{A} \cdot B$	0	1	1	0
Or	$A+B$	0	1	1	1
Nor	$\overline{A+B}$	1	0	0	0
Equivalence	$A \cdot B + \bar{A} \cdot \bar{B}$	1	0	0	1
Not B	\bar{B}	1	0	1	0
If B then A	$A + \bar{B}$	1	0	1	1
Not A	\bar{A}	1	1	0	0
If X then Y	$\bar{A} + B$	1	1	0	1
Nand	$\overline{A \cdot B}$	1	1	1	0
Constant One	1	1	1	1	1

Logic Gates

- An electronic circuit representing a logic function is called a *gate*
- So with electronic circuits that represents And, Or and Not
- We can combine them to build any logic function as a circuit
- To process the signals in the computer

Show YouTube clip

Boolean Algebra

- There are a set of algebraic rules for logic functions
- Set out by George Boole in 'A Calculus of Logic'
- Allows us to reason about logic functions and simplify them...
- Can also use them to show that we can build every logic function if we are given NAND

Boole, 1815-1864

Boolean Algebra

- Already seen how we can build all two-input functions from And, Or and Not
- So if we can build those three functions using NAND then we can build all the functions

Boolean Definitions

- First, set define the action of functions

$$0+0 = 0$$

$$0+1 = 1$$

$$1+0 = 1$$

$$1+1 = 1$$

$$0 \bullet 0 = 0$$

$$0 \bullet 1 = 0$$

$$1 \bullet 0 = 0$$

$$1 \bullet 1 = 1$$

Equivalent to the truth table

Boolean Definitions

- Second, functions for which one input is a variable

$$A+0 = A$$

$$A+1 = 1$$

$$A+A = A$$

$$A+\overline{A} = 1$$

$$A\cdot 0 = 0$$

$$A\cdot 1 = A$$

$$A\cdot A = A$$

$$A\cdot\overline{A} = 0$$

$$\overline{\overline{A}} = A$$

Go through them

Last one is NOT of NOT A

Boolean Definitions

- Third, for more than one variable

$$\begin{array}{lclclcl} A+B & = & B+A & A \cdot B & = & B \cdot A \\ (A+B)+C & = & A+(B+C) & (A \cdot B) \cdot C & = & A \cdot (B \cdot C) \\ (A \cdot B)+(A \cdot C) & = & A \cdot (B+C) & (A+B) \cdot (A+C) & = & A+(B \cdot C) \end{array}$$

Go through them

Boolean Definitions

- Fourth, De Morgan's Theorem

$$\overline{A \cdot B} = \overline{A} + \overline{B} \qquad \overline{A + B} = \overline{A} \cdot \overline{B}$$

Go through them

These rules are what lets us build everything out of NAND gates

Show truth tables on board for these

Logic Gates

- Given a set of NAND gates, we can design any logic circuit we want
- Can get programmable logic chips that are just arrays of NAND gates
- Easier to design using And, Or and Not gates
- As it's *canonical* representation
- And let the computer convert into NAND gates

Hardware Description Language

- Describe the circuit using a *Hardware Description Language*
- Write the hardware as if it were a computer program using a language
- Express how the various AND, OR and NOT gates connect
- Software then generates necessary NAND gates for a *Programmable Logic Device*

Hardware Description Language

- Lots of HDLs about, two common ones are:
 - Verilog
 - VHDL
- We are going to use one that is part of NAND2TETRIS
- This comes with a simulator we can use to experiment

Go demo it...

Designing Logic Circuits

- Often helpful to start by building up the truth table
- Then work out the equations for each output for each line based on the input
- *OR* each of these together for each output
- Then simplify the equations

Simplifying

- Use the algebraic rules etc...
- Look for common sub-equations and move to a separate equation
- Aim is to use as few gates as possible
 - Saves money
 - Reduces propagation delay

Propagation delay is the time taken for a change in the inputs to be reflected in the output of a gate (74LS00 is around 18ns). As gates are combined together the delays add together

Binary Decoder

- Design a logic circuit that can convert a number in binary to a series of discrete signals
- One for each number
- Look at 2-bit decoder
- Two inputs, four outputs

Go draw output on paper

Multiplexer

- Design a circuit that can combine two sets of two inputs (A_1, B_1 and A_2, B_2) into a single set of two outputs (A_0, B_0)
- Based on two selection wires s_1 and s_2
- If s_1 is 1, then output is A_1, B_1
- If s_2 is 1, then output is A_2, B_2
- What if both s_1 and s_2 are 1...

Not necessarily a problem, depends on how the circuit is driven...