

Addition

Steven R. Bagley

Binary Addition

- Build a circuit to add two binary numbers together
- First let's recap how addition works
- Think about the process we do...
- Since we need to build that process in hardware

Addition

$$\begin{array}{r} 1024 \\ 4096 + \\ \hline \end{array}$$

Standard decimal addition

Addition

$$\begin{array}{r} 1024 \\ 4096 + \\ \hline 0 \end{array}$$

Standard decimal addition

Add 4 and 8 get 12 or 2 and carry 1

Addition

$$\begin{array}{r} 1024 \\ 4096 + \\ \hline 0 \\ 1 \end{array}$$

Standard decimal addition

Add 4 and 6 get 10 or 0 and carry 1

Then add 2,9 and 1 to get 12

Addition

$$\begin{array}{r} 1024 \\ 4096 + \\ \hline 20 \\ | \quad | \end{array}$$

Standard decimal addition

Add 4 and 6 get 10 or 0 and carry 1

Then add 2,9 and 1 to get 12 or 2 and carry 1

Addition

$$\begin{array}{r} 1024 \\ 4096 + \\ \hline 5120 \\ | \quad | \end{array}$$

Standard decimal addition

Add 4 and 6 get 10 or 0 and carry 1

Then add 2,9 and 1 to get 12 or 2 and carry 1

Addition

- Add each column together from right
- If bigger than 9, we *carry over* into the next column
- Binary addition is the same, except we carry if the value is greater than one

Binary Addition

$$\begin{array}{r} 1011 \\ 0001 + \\ \hline \end{array}$$

Start on the right add 1 and 1, produces 10 or 0 and carry 1

Binary Addition

$$\begin{array}{rcccc} 1 & 0 & 1 & 1 & \\ 0 & 0 & 0 & 1 & + \\ \hline & & & 0 & \\ & & & 1 & \end{array}$$

Start on the right add 1 and 1, produces 10 or 0 and carry 1

Add 1, 0 and 1 gives 10, or 0 and carry 1

Binary Addition

$$\begin{array}{rcccc} & 1 & 0 & 1 & 1 & & \\ & 0 & 0 & 0 & 1 & + & \\ \hline & & & 0 & 0 & & \\ & & 1 & 1 & & & \end{array}$$

Start on the right add 1 and 1, produces 10 or 0 and carry 1

Add 1, 0 and 1 gives 10, or 0 and carry 1

Add 0 0 and 1 gives 1

Binary Addition

$$\begin{array}{r} 1011 \\ 0001 + \\ \hline 1100 \\ 1 \\ 1 \end{array}$$

Start on the right add 1 and 1, produces 10 or 0 and carry 1

Add 1, 0 and 1 gives 10, or 0 and carry 1

Add 0 0 and 1 gives 1

Adder

- Each column takes in two input bits
- And produces a sum bit and a carry bit
- Can produce a truth table for this...

Adder Truth-Table

A	B	S	C
0	0		
0	1		
1	0		
1	1		

Adder Truth-Table

A	B	S	C
0	0	0	0
0	1		
1	0		
1	1		

Adder Truth-Table

A	B	S	C
0	0	0	0
0	1	1	0
1	0		
1	1		

Adder Truth-Table

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1		


Adder Truth-Table

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Can now start to think about what logic gates can be used to produce these signals

Carry output is straight-forward... AND gate

eXclusive-OR

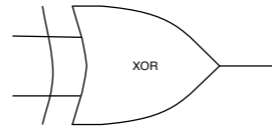

A	B	Result
0	0	0
0	1	1
1	0	1
1	1	0

XOR or EOR gate's truth table looks like this

Symbol used (by engineer's at least) is \oplus

Demo build in NAND2TETRIS


Half-Adder

- Each column takes in two input bits
- And produces a sum bit and a carry bit
- This circuit is known as a half-adder

on the right...

Design Full adder

Equations get more complex

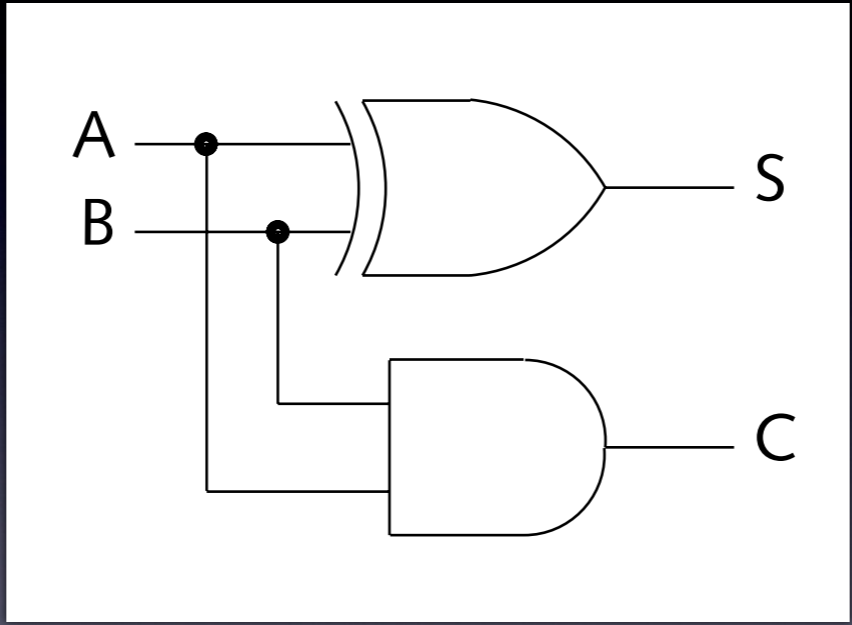

Full Adder

- Half-adder only works to add two bits together
- Sometimes we need to add *three* bits
- When we *carry* a bit
- We also need to be able to provide a carry-in bit from the previous column

Binary Addition

$$\begin{array}{rcccc} 1 & 0 & 1 & 1 & \\ 0 & 0 & 0 & 1 & + \\ \hline & & & 0 & \\ & & 1 & & \end{array}$$

Start on the right add 1 and 1, produces 10 or 0 and carry 1

Add 1, 0 and 1 gives 10, or 0 and carry 1

C	A	B	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0		
1	0	1		
1	1	0		
1	1	1		


Can now start to think about what logic gates can be used to produce these signals

Carry output is straight-forward... AND gate

C	A	B	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full Adder

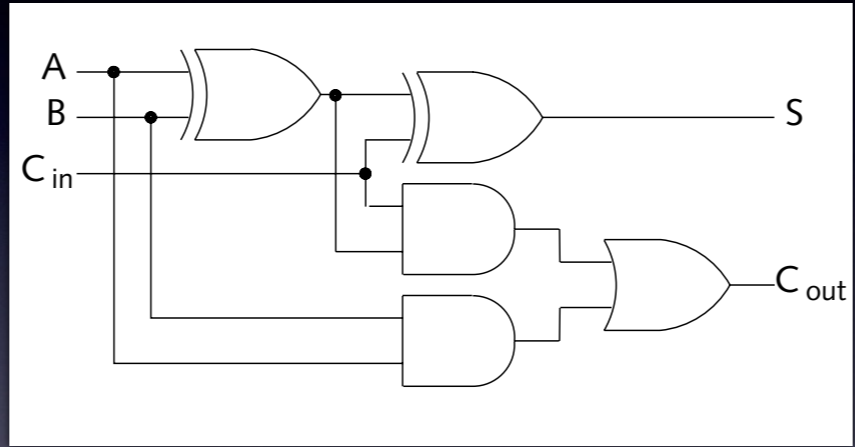
- Circuit described is called a full-adder
- Can combine several of them to add two binary numbers together
- Propagation delay means that it will take some time for the outputs to settle
- So often build adders with several inputs



Chaining Full Adders

- Each adder's C_{out} wired into C_{in} of the next
- n^{th} bit of each input presented to the n^{th} adder's inputs A and B
- First adder's carry input is 0 (usually)
- Last adder's carry output tells if we've overflowed

Ripple Carry Adder

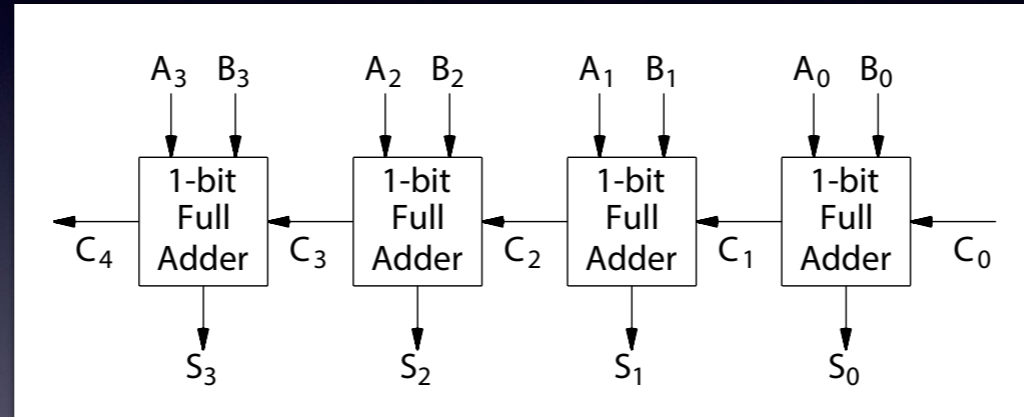


4-bit ripple carry adder

Carry

- Possible for the above Ripple-Carry adder to produce a result bigger than 4-bits
- Hence we still have a carry out
- Adding two n -bit numbers can produce an $(n+1)$ -bit result
- CPUs preserve the carry bit for you

Ripple Carry Adder

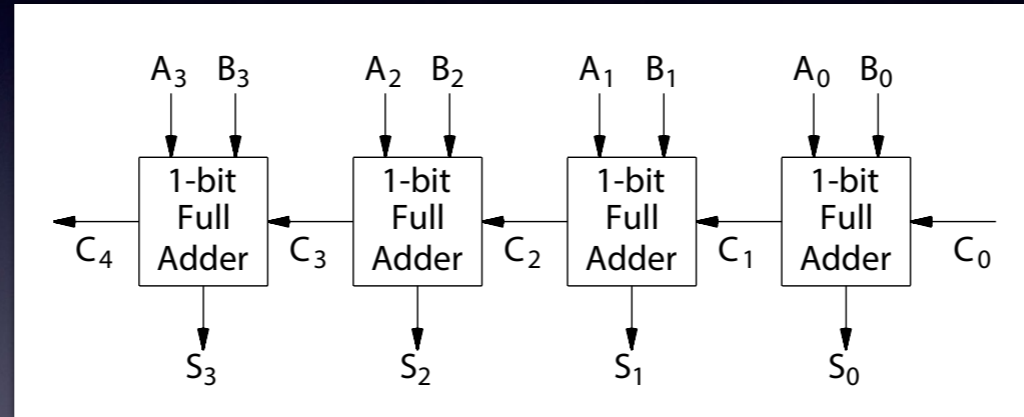

4-bit ripple carry adder