

ALU

Steven R. Bagley

Recap


- Looked at various useful logic functions
- Known as *Combinatorial Logic*
 - Output is a combination of the current input values
- Also *Sequential Logic*
 - Has a time component...
- Fixed functionality — always does the same thing

Mention propagation delay

ALU

- Arithmetic and Logic Unit
- Heart of the CPU performs all the arithmetic and logic operations of the CPU
- Combinatorial Logic
- All CPUs have one, some have several

Apple A7

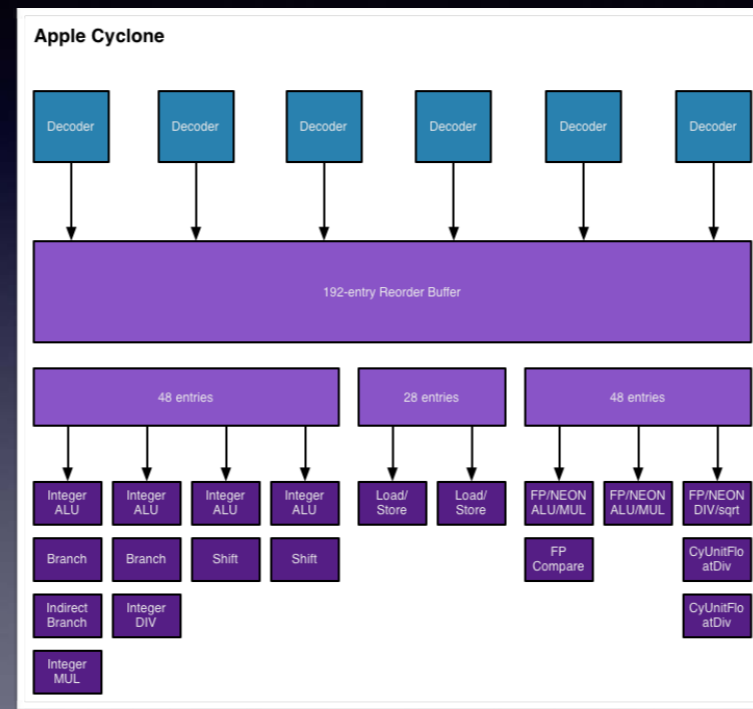


See <http://www.anandtech.com/show/7910/apples-cyclone-microarchitecture-detailed>

By having four ALUs the CPU can do four operations at once, providing they don't rely on the answer from each other

ALU

- Usually considered to have two inputs
- And one output
- These are usually multi-bit
- Use 8-bits in our example...
- Takes the two inputs, performs an operation and produces an output

ALU

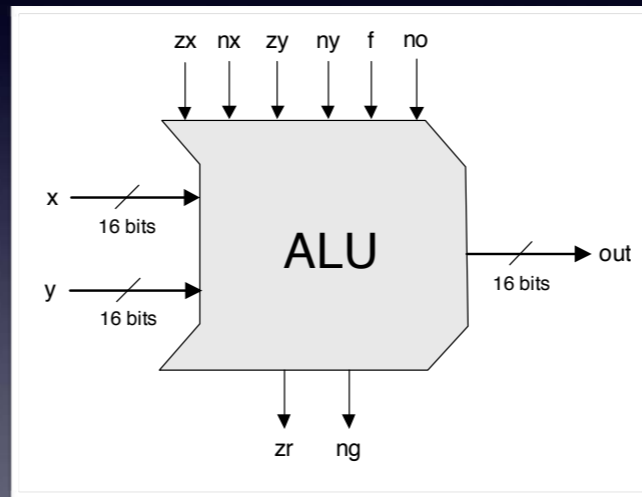


What sort of operations do you want it to do?
Think about the operators we've had in G51PRG

ALU functionality

- ALU functionality is *dynamic* — it can change
 - First, add then later subtract
- Need a mechanism to select which function the ALU performs
- Done by having a set of control pins that *select* what function the ALU is to perform

ALU

 

Now with added function selection pins

ALU functionality

- Lots of possible ALU functions
 - Addition, subtraction, AND/OR/NOT, setting values
- However, we've already seen how some of these operations can be produced in terms of others...
- Want the minimum amount of logic that can perform these tasks...

ALU functionality

- Lots of possible ALU functions
 - Addition, ~~subtraction~~, ~~AND/OR/NOT~~, setting values
- However, we've already seen how some of these operations can be produced in terms of others...
- Want the minimum amount of logic that can perform these tasks...

ALU functionality

- Why minimum?
- Requires less logic gates, means fewer transistors means smaller area on silicon
- Means **cheaper**
- Less *propagation delay*

Propagation Delay

- Our circuit feeds back on itself
- But remember it takes some time for a change in input to reach the output
- So we should really think of the *next* output
- Small, but can add up...
- Particularly at the speeds a computer works at...

Around 5-12ns


ALU functionality

- Why minimum?
- Requires less logic gates, means fewer transistors means smaller area on silicon
- Means **cheaper**
- *Less propagation delay*
- Means **faster**

Worth doing the maths/logic to work out the better circuit :)

Let's look at a sample ALU...

Hack ALU

 

Input	Meaning
zx	if zx then $x = 0$
nx	if nx then $x = \overline{x}$
zy	if zy then $y = 0$
ny	if ny then $y = \overline{y}$
f	if f then $out = x + y$ else $out = x \cdot y$
no	if no then $out = \overline{out}$

From nand2tetris, Stages are sequential in the order shown so X can be zeroed, and inverted...

The output is added or anded then inverted (not)

Explain bitwise and

Show them an equivalent C function for this bit of hardware...

Hack ALU operations

zx	nx	zy	ny	f	no	out
if zx then x = 0	if nx then x = \bar{x}	if zy then y = 0	if ny then y = \bar{y}	if f then out=x+y else out=x*y	if no then out = $\overline{\text{out}}$	f(x,y)=
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	\bar{x}
1	1	0	0	0	1	\bar{y}
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x*y
0	1	0	1	0	1	x y

From nand2tetris, Stages are sequential in the order shown so X can be zeroed, and inverted...

The output is added or anded then inverted (not)

Note: I've used the | as or to distinguish it from the numerical add (with +)

Hack ALU operations

zx	nx	zy	ny	f	no	out
if zx then x = 0	if nx then x = \bar{x}	if zy then y = 0	if ny then y = \bar{y}	if f then out=x+y else out=x*y	if no then out = $\overline{\text{out}}$	f(x,y)=
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	\bar{x}
1	1	0	0	0	1	\bar{y}
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x*y
0	1	0	1	0	1	x y

Fairly obvious what is happening with these here — the f control input is being used to decided between adding and ‘anding’ the input here

Hack ALU operations

zx	nx	zy	ny	f	no	out
if zx then x = 0	if nx then x = \bar{x}	if zy then y = 0	if ny then y = \bar{y}	if f then out=x+y else out=x*y	if no then out = $\overline{\text{out}}$	f(x,y)=
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	\bar{x}
1	1	0	0	0	1	\bar{y}
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x*y
0	1	0	1	0	1	x y

Relatively obvious — using De Morgan's law to produce an OR of the two inputs
 Some of the others are less than straightforward (starting with the second one)


Hack ALU functionality

- From a few relatively simple arrangement of logic gates
- It is possible to create an ALU that can perform many operations
- Not necessarily straightforward to understand how they work — some rely on a blend of mathematical and logical operations to produce the result

Designing ALU

- Start with the functions you want it to do
- Then think about what arrangements of switchable logic functions can provide those functions

Hack ALU

 

Input	Meaning
zx	if zx then $x = 0$
nx	if nx then $x = \overline{x}$
zy	if zy then $y = 0$
ny	if ny then $y = \overline{y}$
f	if f then $out = x + y$ else $out = x \cdot y$
no	if no then $out = \overline{out}$

From nand2tetris, Stages are sequential in the order shown so X can be zeroed, and inverted...

The output is added or anded then inverted (not)

Explain bitwise and

Show them an equivalent C function for this bit of hardware...

Logical Switching

- ALU needs to be able to switch between two sets of values
 - e.g. between x and 0
 - Or between `out` and inverted `out`
- Need a new logic function to handle this, the *muxer*

Muxer

- Short for multiplexor
- Takes two input signals (**A** and **B**)
- And has one output
- The output is the value of either **A** or **B** depending on a third input which we'll call **SEL**(ector)
- Acts like a logic controlled switch
- And, of course, the **SEL** signal can be the result of other logic functions

Show how to create this in the standard way

Then show how to simplify it down into purely NAND gates

Boolean Definitions

- First, set define the action of functions

$$0+0 = 0$$

$$0+1 = 1$$

$$1+0 = 1$$

$$1+1 = 1$$

$$0 \bullet 0 = 0$$

$$0 \bullet 1 = 0$$

$$1 \bullet 0 = 0$$

$$1 \bullet 1 = 1$$

Equivalent to the truth table

Boolean Definitions

- Second, functions for which one input is a variable

$$A+0 = A$$

$$A+1 = 1$$

$$A+A = A$$

$$A+\overline{A} = 1$$

$$A\cdot 0 = 0$$

$$A\cdot 1 = A$$

$$A\cdot A = A$$

$$A\cdot\overline{A} = 0$$

$$\overline{\overline{A}} = A$$

Go through them

Last one is NOT of NOT A

Boolean Definitions

- Third, for more than one variable

$$\begin{array}{lclclcl} A+B & = & B+A & A \cdot B & = & B \cdot A \\ (A+B)+C & = & A+(B+C) & (A \cdot B) \cdot C & = & A \cdot (B \cdot C) \\ (A \cdot B)+(A \cdot C) & = & A \cdot (B+C) & (A+B) \cdot (A+C) & = & A+(B \cdot C) \end{array}$$

Go through them

Boolean Definitions

- Fourth, De Morgan's Theorem

$$\overline{A \cdot B} = \overline{A} + \overline{B} \qquad \overline{A + B} = \overline{A} \cdot \overline{B}$$

Go through them

These rules are what lets us build everything out of NAND gates

Show truth tables on board for these