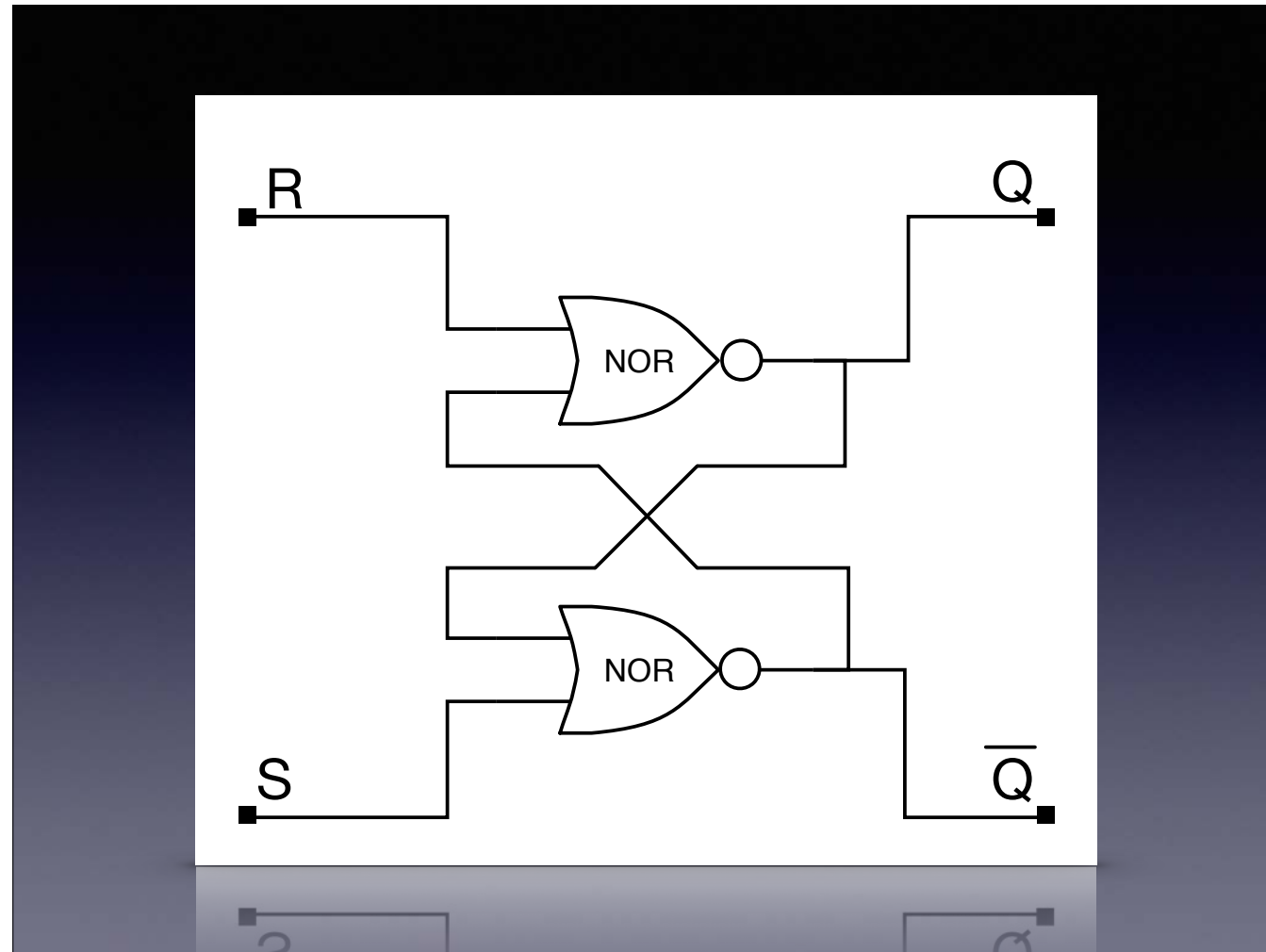


# Sequential Logic


Steven R. Bagley

# Introduction

- Seen some simple logic circuits
  - Adders
  - Multiplexers




What does this circuit do?

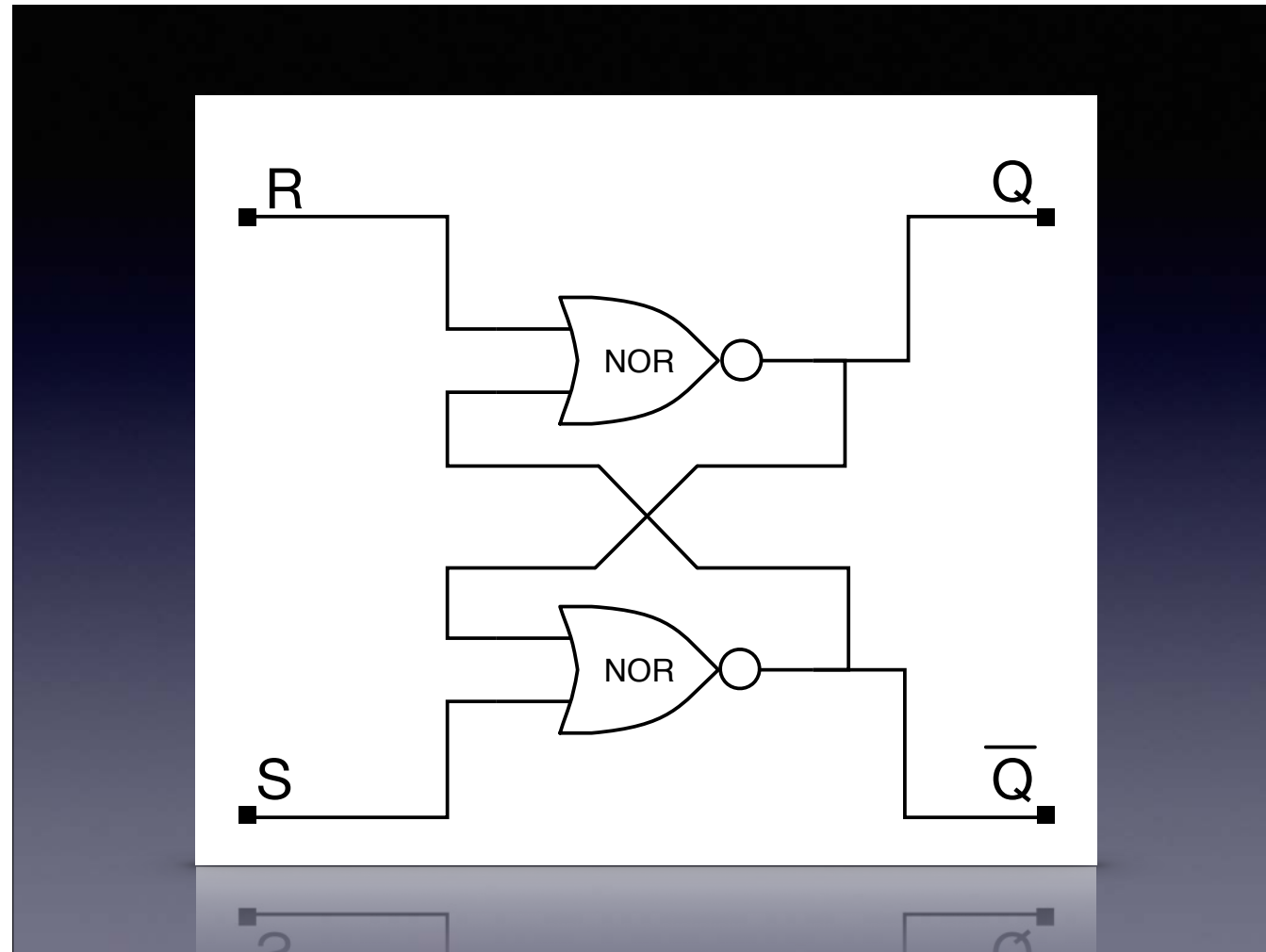

So what about our mystery circuit?

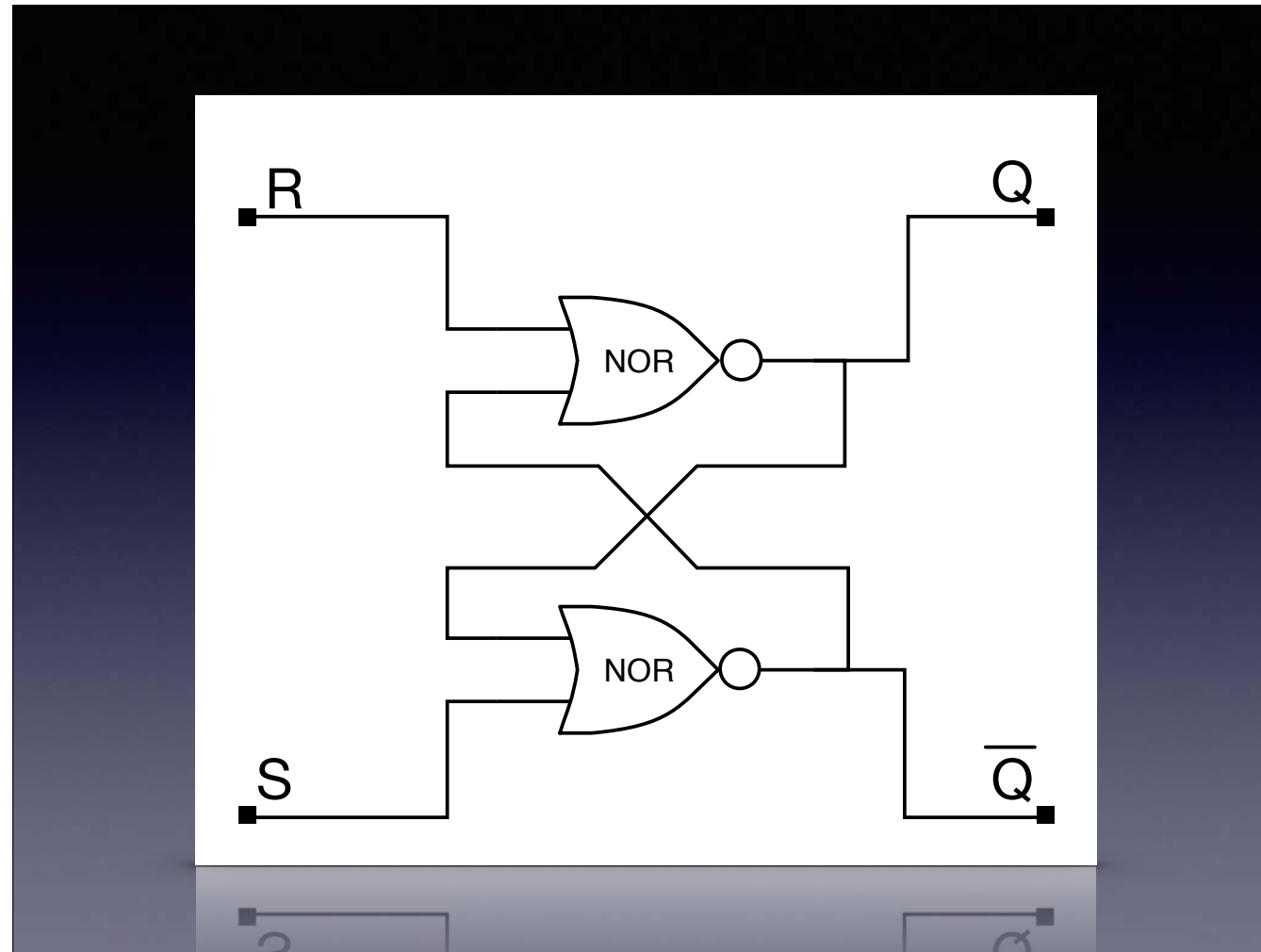Can apply the same thing — but our inputs are connected to our output




So what about our mystery circuit?

Can apply the same thing — but our inputs are connected to our output

Q often used to represent output

Qbar signal is always the opposite of Q

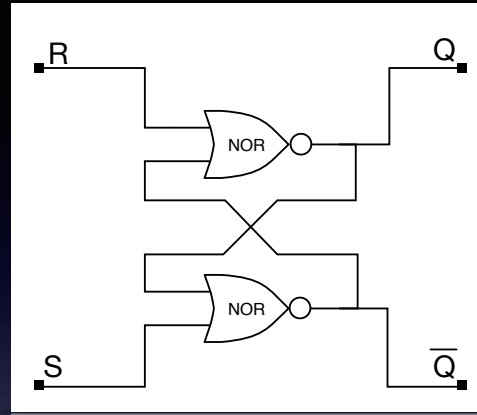

$$Q = \overline{R + \overline{Q}}$$

$$\overline{Q} = \overline{S + Q}$$

So what about our mystery circuit?

Can apply the same thing — but our inputs are connected to our output

Q often used to represent output


Qbar signal is always the opposite of Q

# Propagation

- Our circuit feeds back on itself
- But remember it takes some time for a change in input to reach the output
- So we should really think of the *next*  $Q$  (or  $Q_{\text{NEXT}}$ ) rather in those equations
- Can see this if we look at a simpler example...

And build up a series of truth tables.

# NOT Oscillator

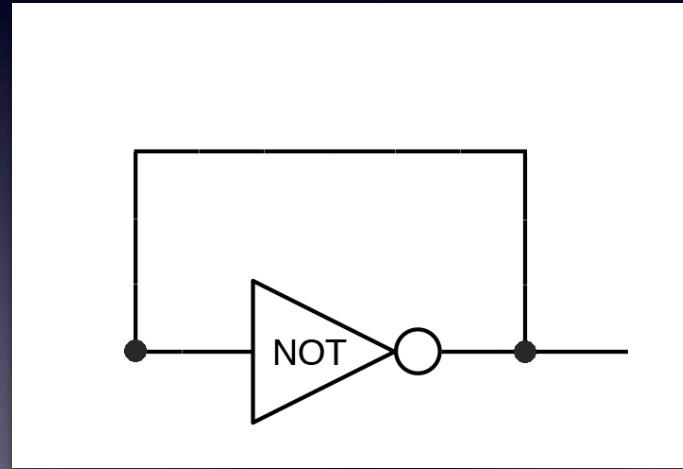


| Input | Output |
|-------|--------|
|-------|--------|

Connecting a NOT gate's output to its input will create an output that oscillates between 0 and 1 (rate determined by the propagation delay)




# NOT Oscillator

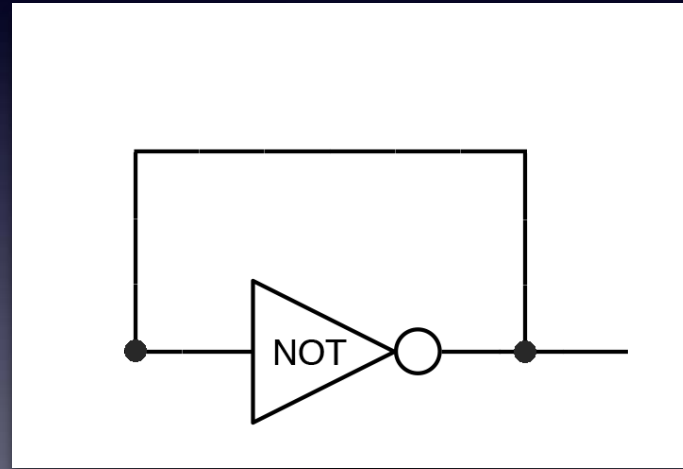

| Input | Output |
|-------|--------|
| 0     | 1      |

Connecting a NOT gate's output to its input will create an output that oscillates between 0 and 1 (rate determined by the propagation delay)


# NOT Oscillator

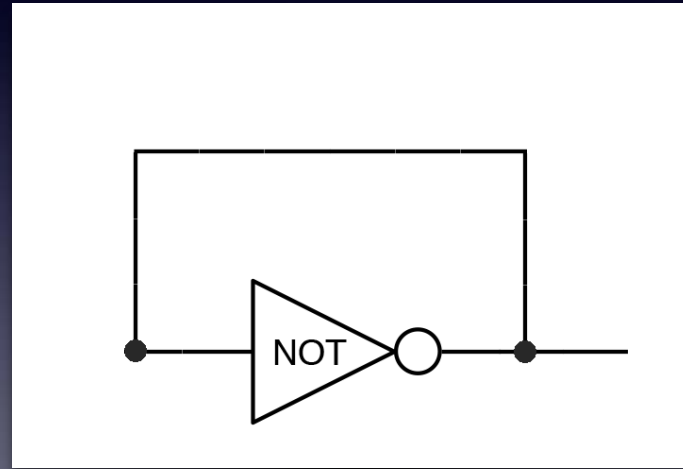

| Input | Output |
|-------|--------|
| 0     | 1      |
| 1     | 0      |

Connecting a NOT gate's output to its input will create an output that oscillates between 0 and 1 (rate determined by the propagation delay)


# NOT Oscillator

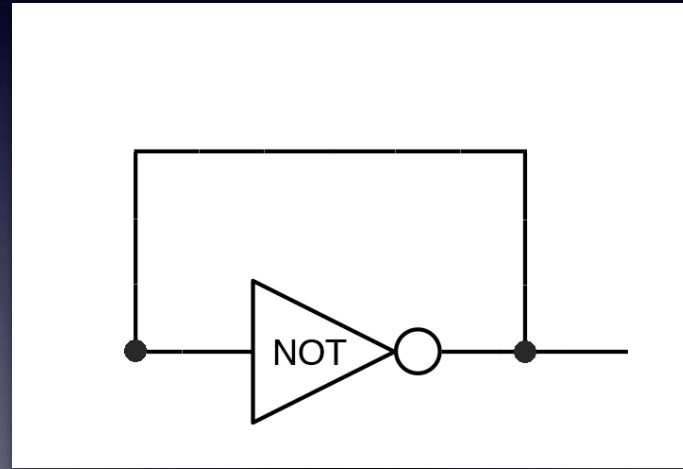

| Input | Output |
|-------|--------|
| 0     | 1      |
| 1     | 0      |
| 0     | 1      |

Connecting a NOT gate's output to its input will create an output that oscillates between 0 and 1 (rate determined by the propagation delay)


# NOT Oscillator

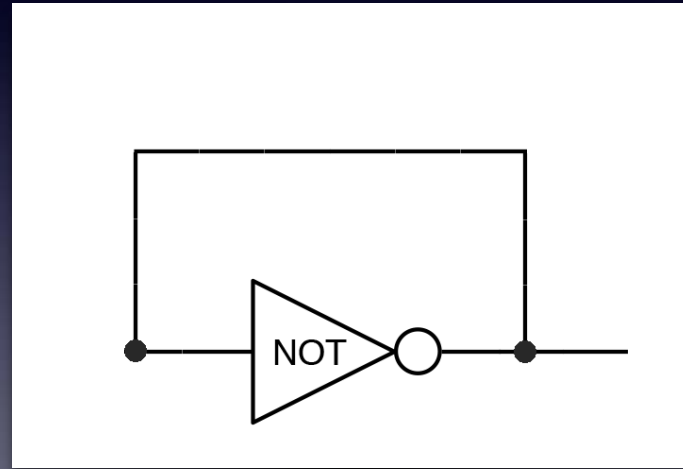

| Input | Output |
|-------|--------|
| 0     | 1      |
| 1     | 0      |
| 0     | 1      |
| 1     | 0      |

Connecting a NOT gate's output to its input will create an output that oscillates between 0 and 1 (rate determined by the propagation delay)

# SR Latch

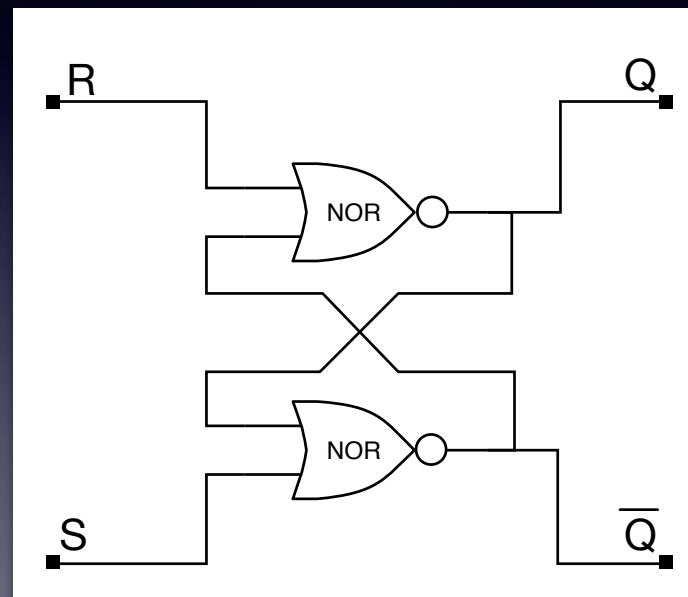


| R | S | Q | $\bar{Q}$ | $Q_{next}$ | $\bar{Q}_{next}$ |
|---|---|---|-----------|------------|------------------|
|---|---|---|-----------|------------|------------------|

When S goes high, the outputs wobble and then Q also goes high

When S then goes low, Q still stays high

Causes Q to remember it is set...

# SR Latch

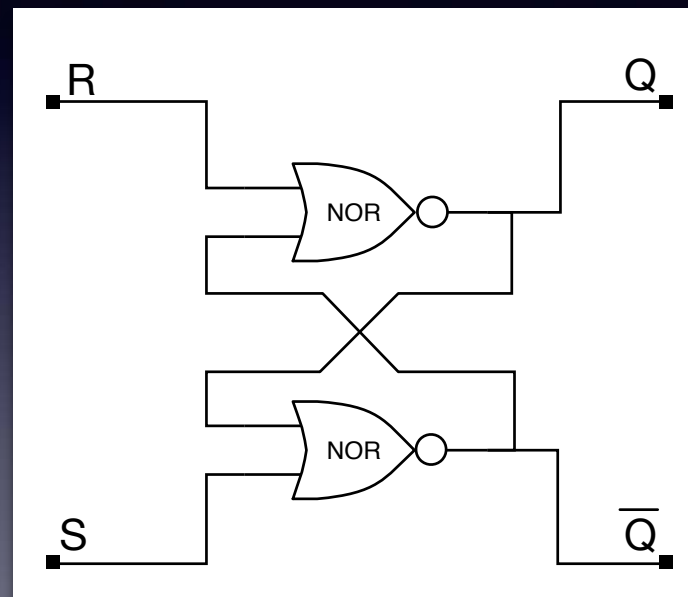


| R | S | Q | $\bar{Q}$ | $Q_{\text{next}}$ | $\bar{Q}_{\text{next}}$ |
|---|---|---|-----------|-------------------|-------------------------|
| 0 | 0 | — | —         | $\bar{Q}$         | $\bar{Q}$               |

When S goes high, the outputs wobble and then Q also goes high

When S then goes low, Q still stays high

Causes Q to remember it is set...

# SR Latch

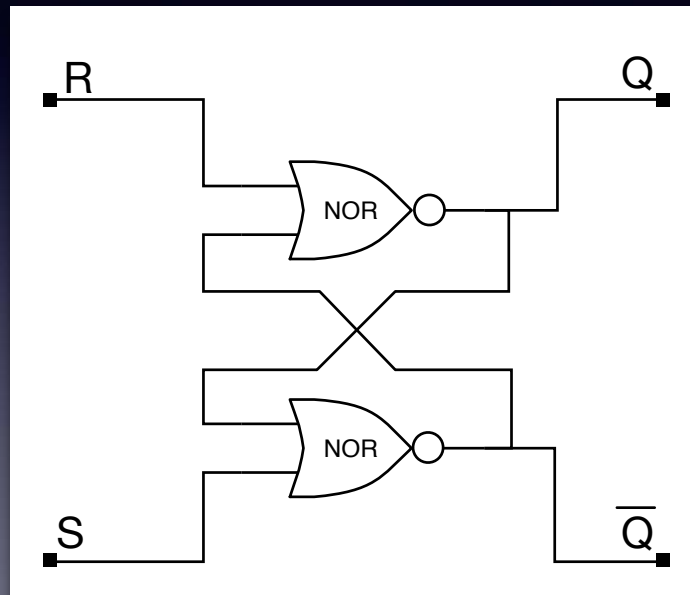


| R | S | Q | $\bar{Q}$ | $Q_{next}$ | $\bar{Q}_{next}$ |
|---|---|---|-----------|------------|------------------|
| 0 | 0 | — | —         | $\bar{Q}$  | $\bar{Q}$        |
| 0 | 1 | Q | $\bar{Q}$ | $\bar{Q}$  | 0                |

When S goes high, the outputs wobble and then Q also goes high

When S then goes low, Q still stays high

Causes Q to remember it is set...

# SR Latch

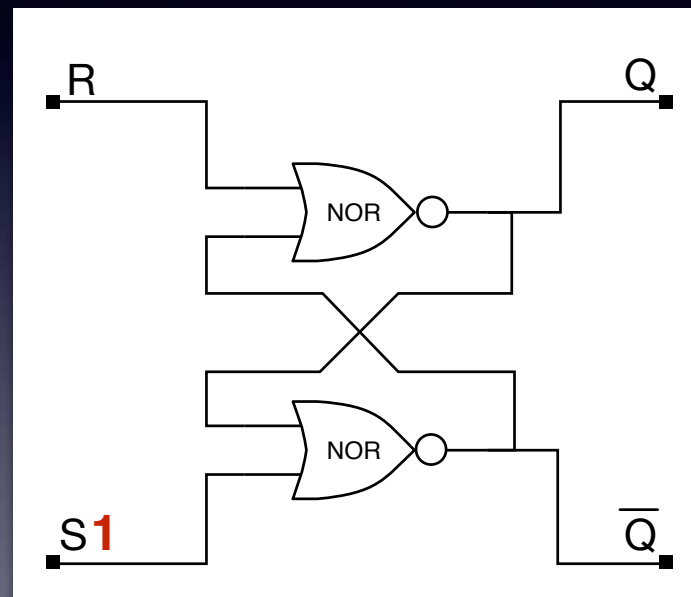

| R | S | Q | $\bar{Q}$ | $Q_{next}$ | $\bar{Q}_{next}$ |
|---|---|---|-----------|------------|------------------|
| 0 | 0 | — | —         | $\bar{Q}$  | $Q$              |
| 0 | 1 | Q | $\bar{Q}$ | $\bar{Q}$  | 0                |


When S goes high, the outputs wobble and then Q also goes high

When S then goes low, Q still stays high

Causes Q to remember it is set...



# SR Latch

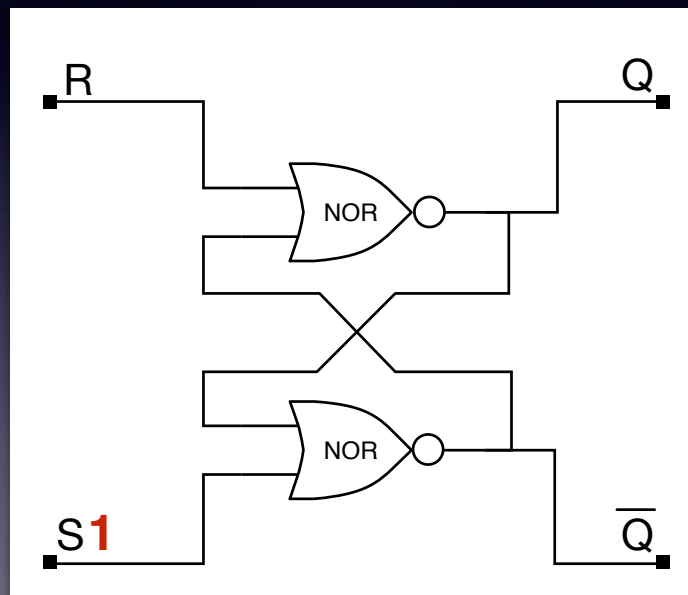


| R | S | Q | $\bar{Q}$ | $Q_{next}$ | $\bar{Q}_{next}$ |
|---|---|---|-----------|------------|------------------|
| 0 | 0 | — | —         | $\bar{Q}$  | $\bar{Q}$        |
| 0 | 1 | Q | $\bar{Q}$ | $\bar{Q}$  | 0                |
| 0 | 1 | Q | 0         | 1          | 0                |

When S goes high, the outputs wobble and then Q also goes high

When S then goes low, Q still stays high

Causes Q to remember it is set...

# SR Latch

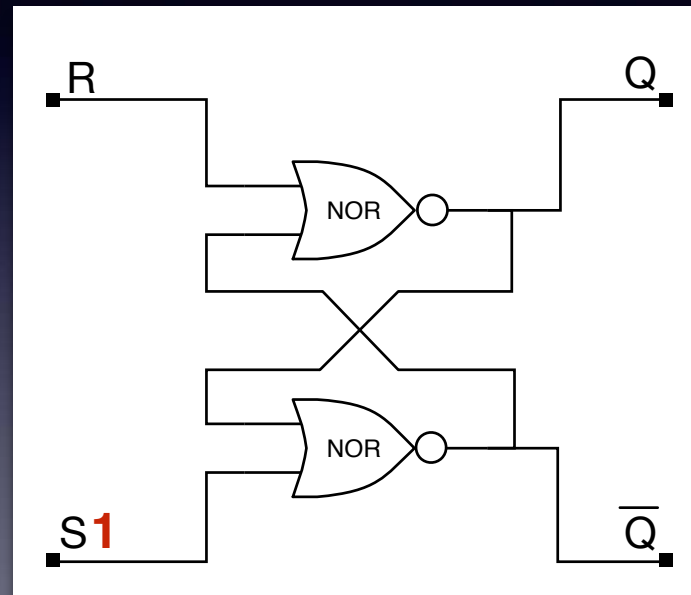


| R | S | Q | $\bar{Q}$ | $Q_{next}$ | $\bar{Q}_{next}$ |
|---|---|---|-----------|------------|------------------|
| 0 | 0 | — | —         | $\bar{Q}$  | $\bar{Q}$        |
| 0 | 1 | Q | $\bar{Q}$ | $\bar{Q}$  | 0                |
| 0 | 1 | Q | 0         | 1          | 0                |
| 0 | 1 | 1 | 0         | 1          | 0                |

When S goes high, the outputs wobble and then Q also goes high

When S then goes low, Q still stays high

Causes Q to remember it is set...

# SR Latch

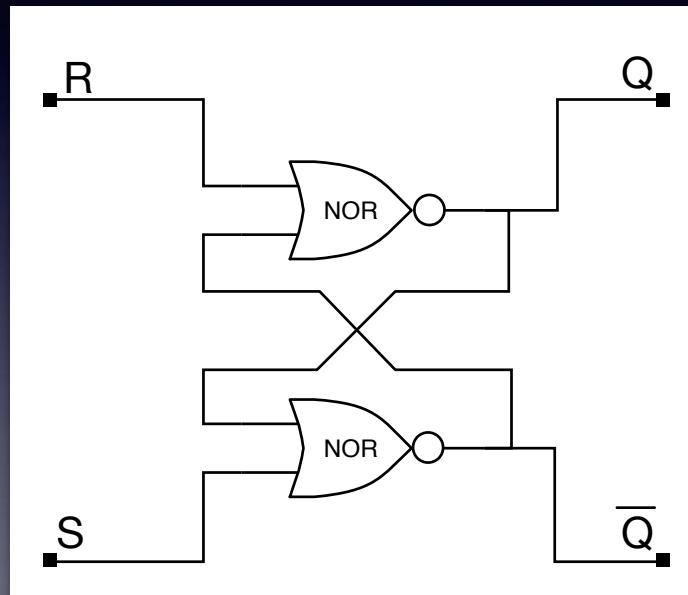


| R | S | Q | $\bar{Q}$ | $Q_{next}$ | $\bar{Q}_{next}$ |
|---|---|---|-----------|------------|------------------|
| 0 | 0 | — | —         | $\bar{Q}$  | $\bar{Q}$        |
| 0 | 1 | Q | $\bar{Q}$ | $\bar{Q}$  | 0                |
| 0 | 1 | Q | 0         | 1          | 0                |
| 0 | 1 | 1 | 0         | 1          | 0                |

When S goes high, the outputs wobble and then Q also goes high

When S then goes low, Q still stays high

Causes Q to remember it is set...

# SR Latch

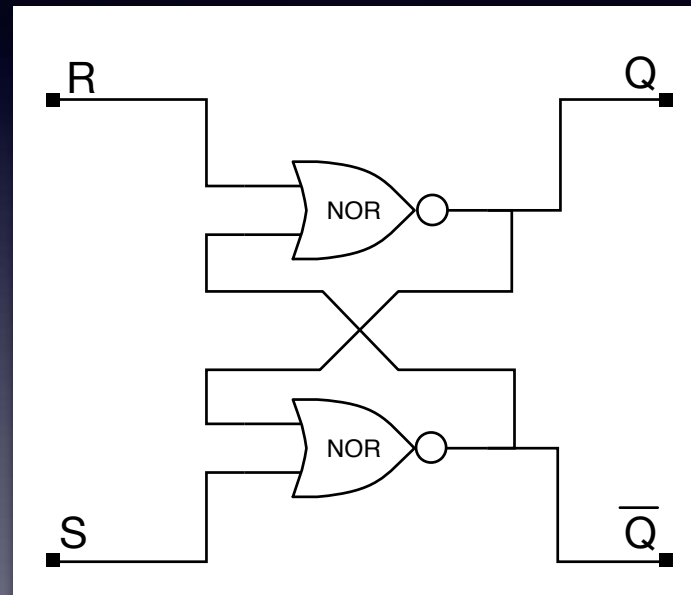


| R | S | Q | $\bar{Q}$ | $Q_{next}$ | $\bar{Q}_{next}$ |
|---|---|---|-----------|------------|------------------|
| 0 | 0 | — | —         | $\bar{Q}$  | $\bar{Q}$        |
| 0 | 1 | Q | $\bar{Q}$ | $\bar{Q}$  | 0                |
| 0 | 1 | Q | 0         | 1          | 0                |
| 0 | 1 | 1 | 0         | 1          | 0                |
| 0 | 0 | 1 | 0         | 1          | 0                |

When S goes high, the outputs wobble and then Q also goes high

When S then goes low, Q still stays high

Causes Q to remember it is set...

# SR Latch

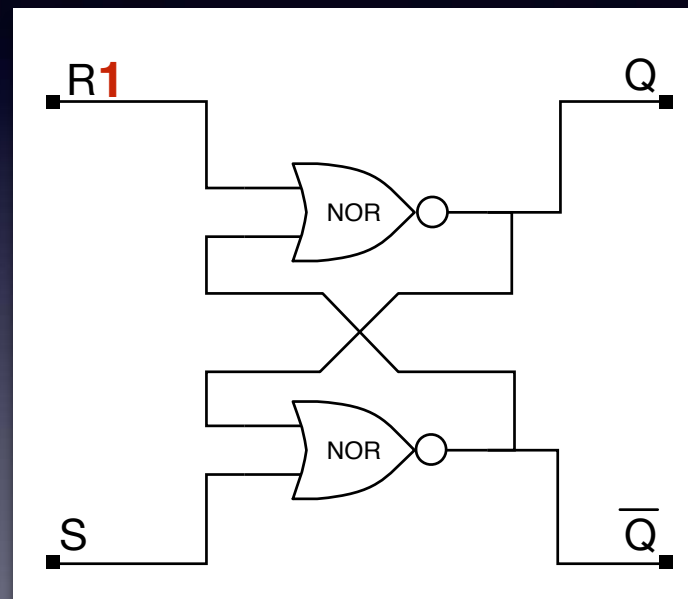


|   |   |   |           |            |                  |
|---|---|---|-----------|------------|------------------|
| R | S | Q | $\bar{Q}$ | $Q_{next}$ | $\bar{Q}_{next}$ |
|---|---|---|-----------|------------|------------------|

When R goes high, the outputs wobble and then Q lies

When R then goes low, Q still stays low

Causes Q to reset to 0

# SR Latch

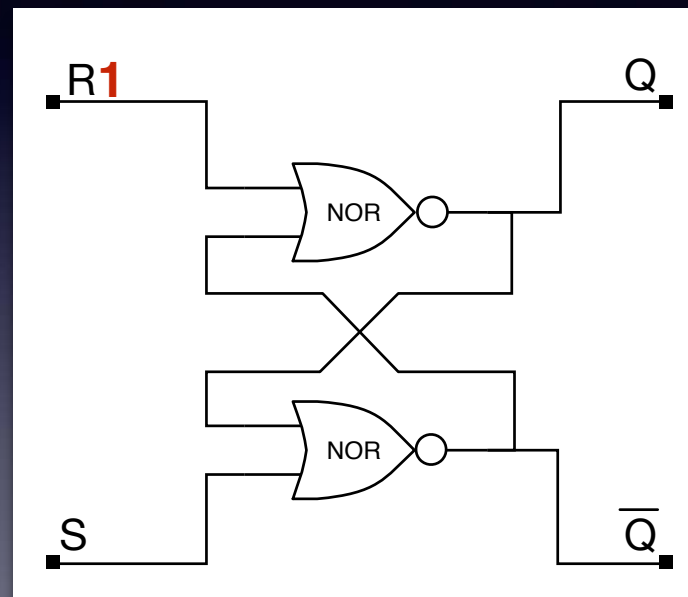


| R | S | Q | $\bar{Q}$ | $Q_{\text{next}}$ | $\bar{Q}_{\text{next}}$ |
|---|---|---|-----------|-------------------|-------------------------|
| 0 | 0 | 1 | 0         | 1                 | 0                       |

When R goes high, the outputs wobble and then Q lies

When R then goes low, Q still stays low

Causes Q to reset to 0

# SR Latch

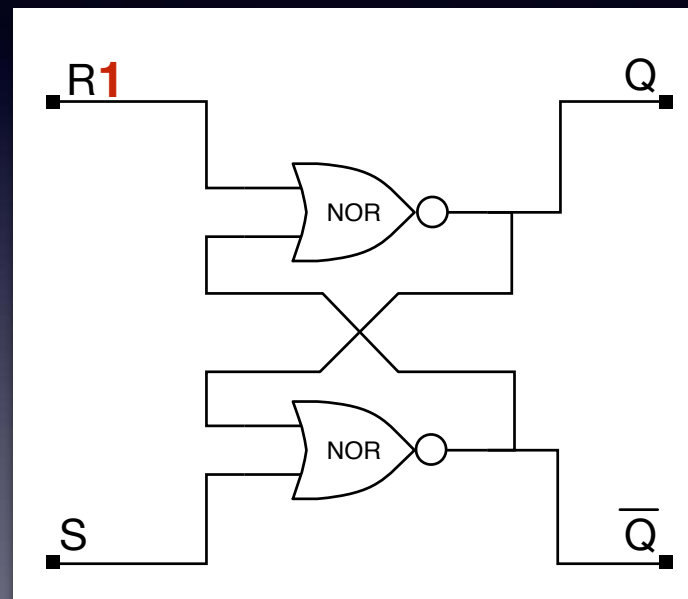


| R | S | Q | $\bar{Q}$ | $Q_{next}$ | $\bar{Q}_{next}$ |
|---|---|---|-----------|------------|------------------|
| 0 | 0 | 1 | 0         | 1          | 0                |
| 1 | 0 | 1 | 0         | 0          | 0                |

When R goes high, the outputs wobble and then Q lies

When R then goes low, Q still stays low

Causes Q to reset to 0

# SR Latch

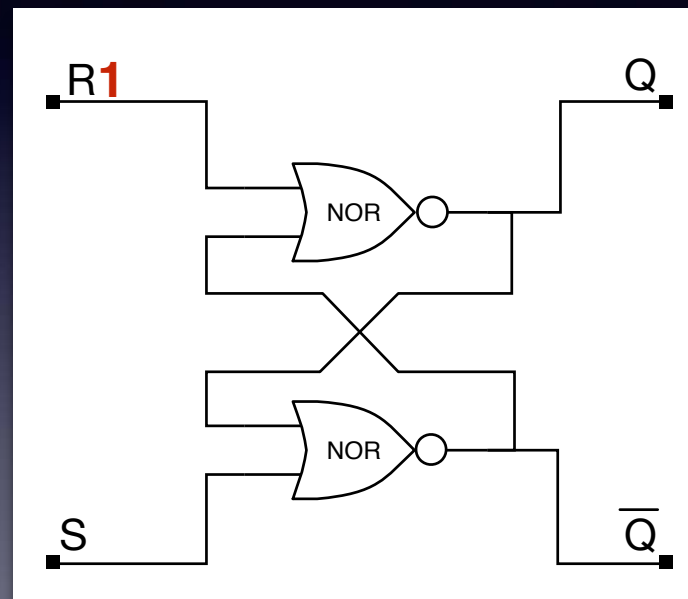

| R | S | Q | $\bar{Q}$ | $Q_{next}$ | $\bar{Q}_{next}$ |
|---|---|---|-----------|------------|------------------|
| 0 | 0 | 1 | 0         | 1          | 0                |
| 1 | 0 | 1 | 0         | 0          | 0                |
| 1 | 0 | 0 | 0         | 0          | 1                |


When R goes high, the outputs wobble and then Q lies

When R then goes low, Q still stays low

Causes Q to reset to 0



# SR Latch

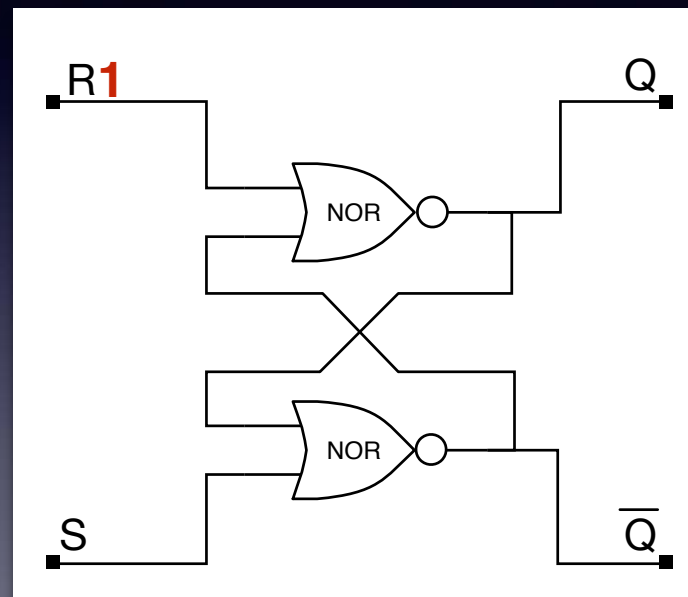


| R | S | Q | $\bar{Q}$ | $Q_{next}$ | $\bar{Q}_{next}$ |
|---|---|---|-----------|------------|------------------|
| 0 | 0 | 1 | 0         | 1          | 0                |
| 1 | 0 | 1 | 0         | 0          | 0                |
| 1 | 0 | 0 | 0         | 0          | 1                |
| 1 | 0 | 0 | 1         | 0          | 1                |

When R goes high, the outputs wobble and then Q lies

When R then goes low, Q still stays low

Causes Q to reset to 0

# SR Latch

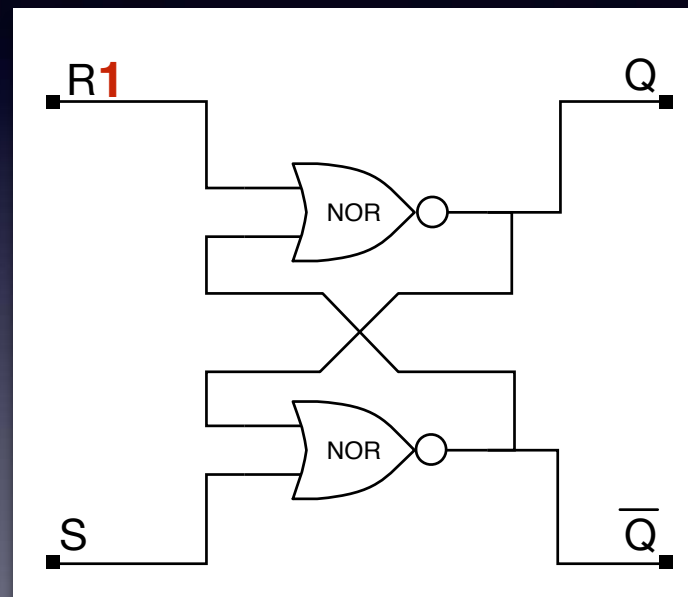

| R | S | Q | $\bar{Q}$ | $Q_{next}$ | $\bar{Q}_{next}$ |
|---|---|---|-----------|------------|------------------|
| 0 | 0 | 1 | 0         | 1          | 0                |
| 1 | 0 | 1 | 0         | 0          | 0                |
| 1 | 0 | 0 | 0         | 0          | 1                |
| 1 | 0 | 0 | 1         | 0          | 1                |
| 0 | 0 | 0 | 1         | 0          | 1                |

When R goes high, the outputs wobble and then Q lies

When R then goes low, Q still stays low

Causes Q to reset to 0

# Storing State

- This circuit remembers things!
- It remembers if its been set, or reset
- Called an SR NOR latch
- But things go wrong if both R and S set...
- Often have additional circuitry to avoid this...

Work through the table to see what happens if R and S both 1, usually delivers

# D Latch

- The D latch is a variation on this that is slightly more useful
- Has a data input (D) and a clock input
- When CLK is high, D goes through to the output
- When CLK is low, output latches last output
- Easy to see how to build this from an SR latch

Show how


$R = \sim D \text{ and } E$

$S = D \text{ and } E$


# Flip-flops

- Latches pass the input to output whenever the CLK input is high
- Flip-flop is a similar circuit but stores the input on the CLK's transition from low to high
- Also sometimes have a clear input to reset the latch/flip-flop

# D-latch D-flip-flop symbol

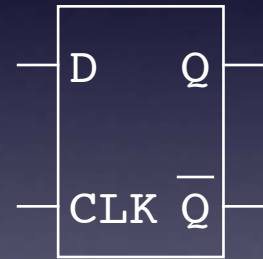

D latch

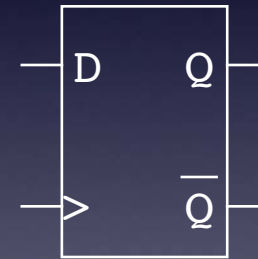

D flip-flop

Often drawn in circuits like this

# Sequential Logic

- Can combine flip-flops with standard combination logic to produce circuits
- These circuits are capable of remembering things
- Also forms the basis of the computer's memory

Draw some examples on paper and talk through them.